
 


Synchronous Logic Blocks

- ▶ Some synchronous logic blocks have standard implementations
 - ▶ Enabled flip-flops
 - ▶ Counters; Binary, Johnson
 - ▶ Shift Registers
 - ▶ Accumulator

Synchronous Logic Blocks

 - ▶ These blocks are distinguished from state machines by very regular behavior.
- ▶ As such, they can be coded in a simplified manner.
- ▶ State machines tend to have more irregular behavior.
- ▶ ~~They~~ are coded in a flexible, general purpose way that makes it natural to express complex and non-regular behavior.




Synchronous Logic Blocks

\\enabled flip-flop, asynchronous reset

```
module en_ff_ar(
    input    clk,
    input    reset_n,
    input    en,
    input    d_in,
    output reg q_out);
    always_ff @ (posedge clk, negedge reset_n)
        if(~reset_n) q_out <= '0;
        else if(en) q_out <= d_in;
endmodule
```


\\enabled flip-flop, synchronous reset
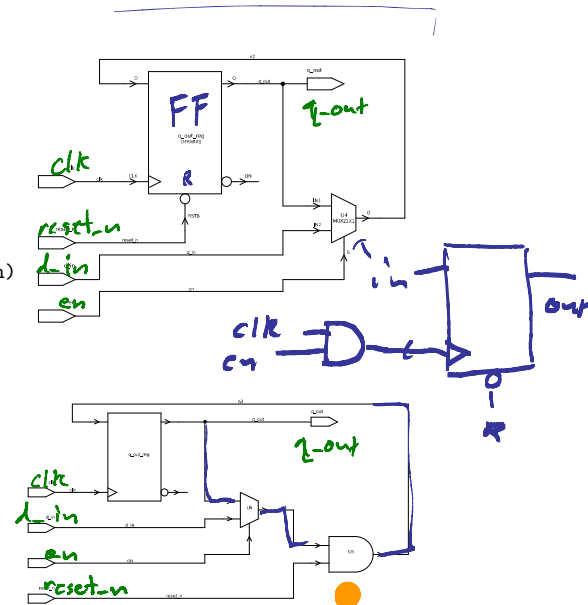
```
module en_ff_sr(
    input    clk,
    input    reset_n,
    input    en,
    input    d_in,
    output reg q_out);
    always_ff @ (posedge clk)
        if(~reset_n) q_out <= '0;
        else if(en) q_out <= d_in;
endmodule
```



Synchronous Logic Blocks
 
```
\\binary counter, enabled, async reset
module bin_cntr_en_ar(
    input      clk,
    input      reset_n,
    input      en,
    output reg [7:0] q_out
);
    always_ff @ (posedge clk, negedge reset_n)
        if(~reset_n) q_out <= '0;
        else if(en)  q_out <= q_out + 1;
endmodule
```




Synchronous Logic Blocks

```

\\Johnson (twisted-ring) counter, async reset
module jhsn_cntr_ar(
    input      clk,
    input      reset_n,
    output reg [3:0] q_out
);
    always_ff @ (posedge clk, negedge reset_n)
    if(~reset_n)
        q_out <= '0;
    else begin
        q_out[0] <= ~q_out[3];
        q_out[1] <= q_out[0];
        q_out[2] <= q_out[1];
        q_out[3] <= q_out[2];
    end //else
endmodule

```

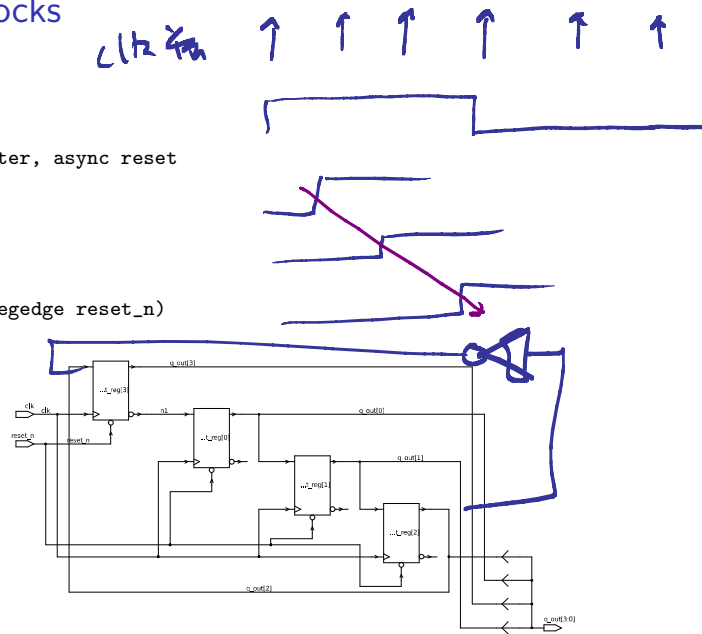


Synchronous Logic Blocks

```


module multi_reg_ar #(parameter WIDTH=8)(
//a multipurpose register
input          clk,          //clk
input          reset_n,      //async reset
input          en,           //enable
input          shift,        //shift=1, load=0
input          l_or_rt,      //left=1, right=0
input          din_left,     //data into MSB
input          din_right,    //data into LSB
input          [WIDTH-1:0] d_in, //parallel inputs
output reg [WIDTH-1:0] q_out //parallel outputs
);
always_ff @ (posedge clk, negedge reset_n)
if(~reset_n)
q_out <= '0; //clear register
else if(en)
if(~shift) q_out <= d_in; //broadside load
else
if (l_or_rt) //left
q_out <= {q_out[WIDTH-2:0], din_left }; //shift left
else
q_out <= {din_right, q_out[WIDTH-1:1]}; //shift right
endmodule

```

 

Synchronous Logic Blocks

```
module multi_reg_ar(  
    .....  
always_ff @ (posedge clk, negedge reset_n)  
    if(~reset_n)  
        q_out <= '0;          //clear register  
    else if(en)  
        if(~shift) q_out <= d_in; //broadside load  
        else  
            if (l_or_rt)  
                q_out <= {q_out[WIDTH-2:0], din_left }; //shift left  
            else  
                q_out <= {din_right, q_out[WIDTH-1:1]}; //shift right
```

 


Synchronous Logic Blocks


```

module accumulator (
  //a simple accumulator or summer with
  //both sync and async resets
  //sync reset operates independent of en
  input      clk,      //clk
  input      reset_n,  //async reset
  input      s_reset,  //sync reset
  input      en,       //enable
  input  [7:0] d_in,   //parallel inputs
  output reg [7:0] q_out //parallel outputs
);
always_ff @ (posedge clk, negedge reset_n)
  if(~reset_n)
    q_out <= '0;    //async clear
  else if(s_reset)
    q_out <= '0;    //sync clear
  else if(en)
    q_out <= q_out + d_in; //accumulate
endmodule

```

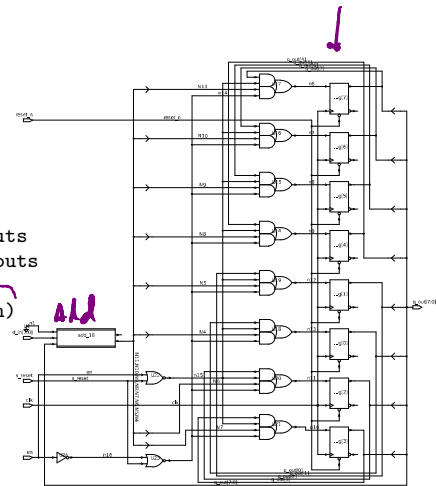

Clock Dividers !

 

Quiz:

1) $=$, $==$, $>$, $!=$ }

2) for ()

3) case, if

4) always : sequential logic

5) initial, #5, wait

6) Grad Students: Presentation Topics