

Sequential Logic


- ▶ Outputs are a reflection of past state values
 - ▶ Flip-flops and latches hold state
- ▶ Only certain input changes cause an change in state
 - ▶ Sensitivity only to clock and reset

```
module reg8 (
    input      clk,
    input      reset_n,
    input [7:0] d_in,
    output reg [7:0] q_out,
);
always_ff @ (posedge clk, negedge reset_n)
    if (~reset_n) q_out <= '0;
    else          q_out <= d_in;
endmodule
```

System Verilog

- ▶ `always_ff` gives clear intent that flip-flops are to be inferred
- ▶ `always_ff` must still include sensitivity list for clock and reset
- ▶ Nonblocking assignment is used under `always` for sequential logic


Sequential Logic

 

```

module reg8 (
    input      clk,
    input      reset_n,
    input [7:0] d_in,
    output reg [7:0] q_out
);
    always_ff @ (posedge clk, negedge reset_n)
    [ if(~reset_n) q_out <= '0;
      else        q_out <= d_in;
    ]
endmodule

```

 

Sequential Logic

- ▶ An asynchronous input such as reset_n changes the state of the flip-flops independent of the sequential trigger.
- ▶ These flip-flops have a level-sensitive, asynchronous reset.
- ▶ The reset signal is made dominant by using the if.
- ▶ Clock input is not tested by an if, async inputs are
- ▶ if-else tests must come before the clocked logic
- ▶ Since reset_n is level sensitive, why do we look at the falling edge?

```
module reg8 (  
    input      clk,  
    input      reset_n,  
    input [7:0] d_in,  
    output reg [7:0] q_out  
);  
always_ff @ (posedge clk, negedge reset_n)  
→ if(~reset_n) q_out <= '0;  
  else      q_out <= d_in;  
endmodule
```




Sequential Logic

- How would it work if we coded this way?... Busted, that's how!

```
module reg8 (  
    input      clk,  
    input      reset_n,  
    input [7:0] d_in,  
    output reg [7:0] q_out  
);  
always_ff @ (posedge clk, reset_n)  
    if (~reset_n) q_out <= '0;  
    else          q_out <= d_in;  
endmodule
```

Not Asynch.
Reset.

 


q-out reset correctly
by reset_n = 0

process woke up with
change in reset_n. Then
reset_n was 1, so q-out
gets reAssigned to d-in.
(Error!)

Sequential Logic
 
```
module reg_en4 (  
    input        clk,  
    input        reset_n,  
    input        en,  
    input  [3:0] d_in,  
    output reg [3:0] q_out  
);  
    always_ff @ (posedge clk)  
    if(~reset_n) q_out <= '0;  
    else if(en)  q_out <= d_in;  
endmodule
```




- ▶ Fully synchronous logic evaluates only on the clock edge
- ▶ What is the difference in this register and the last one?
- ▶ Why isn't `reset_n` and `en` in the sensitivity list?

Sequential Logic

```

module reg_en4 (
    input      clk,
    input      reset_n,
    input      en,
    input  [3:0] d_in,
    output reg [3:0] q_out
);
    always_ff @ (posedge clk)
        if (~reset_n) q_out <= '0;
        else if(en)   q_out <= d_in;
endmodule

```

 

What's going on here?


Sequential Logic

- ▶ What about latches?
 - ▶ Latches are not Registers or Flip-flops
 - ▶ Don't ever confuse the two
 - ▶ We will model transparent latches
 - ▶ Latches combine combo logic with sequential logic
 - ▶ Transparent: pass in to out without sequential trigger (combo logic)
 - ▶ Latched: input is stored (sequential logic)

Sequential Logic

► Modeling a latch
 
```
module latch (  
    input    d, en,  
    output   reg q);  
  
    always_latch  
        if (en) q <= d; //transparent latch  
  
endmodule
```



always @ (en)

