

# Hardware Description Languages

## Introduction and Combinational Logic

Joe Crop

Oregon State University

ECE 271

# Outline

- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic
- 3 Structural Modeling
- 4 Sequential Logic
- 5 Finite State Machines
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary

# Outline


- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic
- 3 Structural Modeling
- 4 Sequential Logic
- 5 Finite State Machines
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary

# What is an HDL?

A Programming language that describes hardware.

# Why HDL?

 1.) Schematics can get large and complicated.



# Why HDL?

2.) The ability to simulate is imperative.



# Why HDL?


3.) Logic minimization and optimization are a pain.

## Beginning Mapping Optimizations (Ultra High effort)

Beginning Mapping Optimizations (Ultra High effort)					
ELAPSED		WORST NEG TOTAL NEG DESIGN			
TIME	AREA	SLACK	SLACK	RULE	COST
0:00:18	372324.0	0.00	0.0		0.6
0:00:19	372324.0	0.00	0.0		0.6
0:00:21	356715.6	0.00	0.0		34.4
0:00:23	356836.8	0.00	0.0		0.0
0:00:24	355791.0	0.00	0.0		0.0
0:00:28	355689.0	0.00	0.0		31.1
0:00:33	355379.1	0.00	0.0		0.0
Optimization Complete					

# Why HDL?

4.) Faster design time is needed.

 



# Types of HDLs

- Verilog
- VHDL
- System-C
- Bluespec
- C/C++
- Matlab

# Modules

Definition: A block of hardware with inputs and outputs.

Examples:

- AND gate
- multiplexer
- Adder
- CPU

# VHDL/Verilog Comparison

## VHDL

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3
4  entity gates is
5      port(in1, in2: in STD_LOGIC;
6           out1: out STD_LOGIC);
7  end;
8
9  architecture synth of gates is
10     signal in1_b: STD_LOGIC;
11 begin
12     in1_b <= not in1;
13     out1 <= in1_b and in2;
14 end
15
16

```


## Verilog

```

1  module gates(in1, in2, out1);
2
3      input  in1;
4      input  in2;
5      output out1;
6
7      wire in1_b;
8
9      assign in1_b = ~in1;
10     assign out1 = in1_b & in2;
11
12 endmodule

```

# Typical Design Cycle

- 1 Concept
  - 2 Design
  - 3 Simulate
  - 4 Synthesize
  - 5 Implement
  - 6 Sign-off
- 

# Outline

- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic**
- 3 Structural Modeling
- 4 Sequential Logic
- 5 Finite State Machines
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary

# Bitwise Operators


operator	function
$\sim$	NOT
$*, /, \%$	Multiply, Divide, Modulo
$<<, >>$	Logical Shift Left, Right
$<<<, >>>$	Arithmetic Shift Left, Right
$<, <=, >, >=$	Relative Comparison
$==, !=$	Equality Comparison
$\&$	AND
$\&\sim$	NAND
$\wedge$	XOR
$\wedge\sim$	XNOR
$ $	OR
$\sim $	NOR
$?:$	Conditional

# Bitwise Operators: Example

## gates.v


```
1  module gates( a, b, y1, y2, y3, y4, y5);
2      input  a;
3      input  b;
4      output y1;
5      output y2;
6      output y3;
7      output y4;
8      output y5;
9
10     assign y1 = a & b;           // AND
11     assign y2 = a | b;           // OR
12     assign y3 = a ^ b;           // XOR
13     assign y4 = ~(a & b);        // NAND
14     assign y5 = ~(a | b);        // NOR
15 endmodule
```

# Buses

 
 
## Buses of wires

```
1 module gates(in1, in2, out1);
2
3   input  [0:2] in1;
4   input  [2:0] in2;
5   output [0:2] out1;
6
7   wire  [0:2] in1_b;
8
9   assign in1_b = ~in1;
10  assign out1 = in1_b & in2;
11
12 endmodule
```





# Comments

## Comments in Verilog

```
1  module gates( a, y);  
2      input  a;  
3      output y;  
4  
5      /* A block coment in Verilog  
6         * consists of either C/C++  
7         * style comment statements  
8         * */  
9  
10     assign y1 = a & b;      // an and gate  
11  
12 endmodule
```


# Reduction Operators

## Buses of wires

```



1  module gates( a, b, y1, y2, y3, y4, y5);
2      input  [3:0] a;
3      input  b;
4      output y1;
5      output y2;
6      output y3;
7      output [1:0] y4;
8      output y5;
9
10     assign y1 = a[0] & b;
11     assign y2 = a[1] | b;
12     assign y3 = a[2] ^ b;
13     assign y4 = ~(a[1:2] & b);
14     assign y5 = ~(a[3] | b);
15 endmodule

```

 


# Multiplexers
  
## Multiplexers using the Conditional operator



```
1 module mux( in_0, in_1, sel, y);  
2     input  in_0;  
3     input  in_1;  
4     input  sel;  
5     output y;  
6  
7     assign y = sel ? in_1 : in_0;  
8  
9 endmodule
```

// A simple MUX

 

# Internal Variables

## Internal Variables

```
1 module gates ( a, b, y );
2   input  a;
3   input  b;
4   output y;
5
6   /* an internal "variable" */
7   wire var_or;
8
9   assign var_or = a | b;      // OR
10  assign y = a & var_or;      // AND
11 endmodule
```



# Formatting Numbers

- Format: (# of bits) (base) (value)
  - 3'b101 = binary 101
  - 8'b101 = binary 00000101
  - 3'd6 = decimal (binary 110)
  - 8'hAB = hexadecimal (binary 10101011)
  - 6'o42 = octal (binary 100010)
- Things to (almost) never do:
  - 0'b11 = 000...0011
  - 42 = 000...0101010
  - 4'bz = high-impedance (zzzz)
  - 4'bx = not defined (xxxx)

# Tristate Buffers


## Example

```
1 module tristate( in, enable, y);  
2   input in;  
3   input enable;  
4   output y;  
5  
6   assign y = sel ? in : 1'bz;      // A tristate buffer  
7  
8 endmodule
```

# Bit Swizzling

More commonly known as concatenation

```
1  module gates(in1, in2, out1);
2
3  input  [0:2] in1;
4  input  [2:0] in2;
5  output [0:2] out1;
6
7  wire  [0:2] in1_b;
8
9  assign in1_b = {in1[0:1], in2[2]};
10 assign out1 = in1_b & in2;
11
12 endmodule
```



# Simulating Delays


## Example

```
1  module gates ( a, b, y1, y2, y3, y4, y5);
2      input  a;
3      input  b;
4      output y1;
5      output y2;
6      output y3;
7      output y4;
8      output y5;
9
10     assign #2 y1 = a & b;           // AND
11     assign #3 y2 = a | b | y1;      // OR
12     assign #1 y3 = a ^ b;          // XOR
13     assign #1 y4 = ~(a & b);        // NAND
14     assign #1 y5 = ~(a | b);        // NOR
15 endmodule
```


 
# Feedback

- Please give me your feedback
  - Email: [cropj@eecs.oregonstate.edu](mailto:cropj@eecs.oregonstate.edu)
  - Text: (541) 250-0253
  - Twitter: @JoeCrop



# Outline

- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic
- 3 Structural Modeling**
- 4 Sequential Logic
- 5 Finite State Machines
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary

# Structural Modeling

*Behavioral Modeling*: Describing a module in terms of inputs and outputs.

*Structural Modeling*: Describing a module in terms of how it is composed of sub-modules.

# A Simple Structure

## Example

```


1  module mux4( in_00, in_01, in_10, in_11 sel, y);
2      input  in_00, in_01, in_10, in_11;
3      input  [1:0] sel;
4      output y;
5
6      assign wire low, high;
7
8      mux LOWMUX(in_00, in_01, sel[0], low);
9      mux HIGHMUX(in_10, in_11, sel[0], high);
10     mux FINALMUX(low, high, sel[1], y);
11 endmodule // mux4
12
13 module mux( in_0, in_1, sel, y);
14     input  in_0, in_1, sel;
15     output y;
16
17     assign y = sel ? in_1 : in_0;
18 endmodule // mux

```

*Handwritten notes:*

- Line 6: ~~assign~~ wire low, high;
- Line 8: LOWMUX (circled in orange)
- Line 9: HIGHMUX (circled in orange)
- Line 10: FINALMUX (circled in orange)
- Line 13: mux (circled in orange)
- Line 14: in\_0, in\_1, sel (circled in orange)
- Line 17: assign y = sel ? in\_1 : in\_0; (circled in orange)
- Line 18: endmodule // mux (circled in orange)

 *Handwritten note at the bottom:* // A simple MUX



# The Correct way to do it!

## Example

```

1 module mux4( in_00, in_01, in_10, in_11 sel, y);
2     input  in_00, in_01, in_10, in_11;
3     input  [1:0] sel;
4     output y;

```

```

6     wire [3:0] low, high;

```

```

8     mux LOWMUX(

```

```


```

```

9         .in_0

```

```

10        .in_1

```

```

11        .sel

```

```

12        .y

```

```

13

```

```

14

```

```

15     mux HIGHMUX(

```

```

16         .in_0

```

```

17         .in_1

```

```

18         .sel

```

```

19         .y

```

```

20     );

```

global

local

# Outline

- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic
- 3 Structural Modeling
- 4 Sequential Logic**
- 5 Finite State Machines
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary


# Registers (DFF)

## Positive Edge

```

1 module flop(clk, d, q);
2   input clk;
3   input d;
4   input out q;
5
6   reg q;
7
8   always @(posedge clk)
9     q <= d;
10
11 endmodule //flop

```

 

## Negative Edge

```

1 module neg_flop(clk, d, q);
2   input clk;
3   input d;
4   input q;
5
6   reg q;
7
8   always @(negedge clk)
9     {
10       begin
11         q <= d;
12       end
13     }
14 endmodule //neg_flop

```



# Resettable Registers (DFFR)

## Example

```

1  module flopr(clk, d, q, reset);
2      input clk, reset;
3      input [0:1] d;
4      input out [0:1] q;
5
6      reg [1:0] q;
7
8      always @(posedge clk) //synchronous reset
9          if(reset) q[0] <= 0;
10         else      q[0] <= d[0];
11
12         always @(posedge clk, posedge reset) //asynchronous reset
13             if(reset) q[0] <= 0;
14             else      q[0] <= d[0];
15
16     endmodule //flopr

```

  



# Enable Registers (DFFE)


## Example

```
1  module flope(clk, d, q, reset, en);
2      input  clk, reset, en, d;
3      output q;
4
5      reg q;
6
7      always @(posedge clk, posedge reset) //asynchronous reset
8          begin
9              if(reset)
10                 begin
11                     q <= 0;
12                 end
13                 else if(en)
14                     begin
15                         q <= d;
16                     end
17                 end
18 endmodule //flope
```

# Multiple Registers

## Example

```
1  module flop(clk, d, q);  
2      input  clk, d;  
3      output q1;  
4  
5      reg q0, q1;  
6  
7      always @(posedge clk)  
8          begin  
9              q0 <= d;  
10             q1 <= q0;  
11         end  
12     endmodule //flop
```



# Latches

Transparent when clock is high.

## Example

```
1  module latch(clk, d, q);
2      input  clk, d;
3      output q;
4
5      reg q;
6
7      always @(clk, d) //sensitivity list
8          if(clk) q <= d;
9
10 endmodule //latch
```

```
module pulse_generator (d, clk, op);
```

```
input d, clk;
```

```
output op;
```

```
reg op;
```

```
reg v1, v2;
```

```
always @(posedge clk)
```

```
begin
```


```
  v1 <= d;
```

```
  v2 <= v1;
```

```
  op <= v1 & ~v2;
```

```
end
```

```
endmodule
```

 

# More Cool stuff

- Case Statements (4.5.1)
- Combinational if/else (4.5.2)
- Blocking / Non-Blocking Assignments (4.5.4)

# Feedback

- Please give me your feedback
  - Email: [cropj@eecs.oregonstate.edu](mailto:cropj@eecs.oregonstate.edu)
  - Text: (541) 250-0253
  - Twitter: @JoeCrop

# Outline

- 1 Hardware Description Languages (HDL)
- 2 Combinational Logic
- 3 Structural Modeling
- 4 Sequential Logic
- 5 Finite State Machines**
- 6 Parameterized Modules
- 7 Testbenches
- 8 Summary

# Feedback

- Please give me your feedback
  - Email: [cropj@eecs.oregonstate.edu](mailto:cropj@eecs.oregonstate.edu)
  - Text: (541) 250-0253
  - Twitter: @JoeCrop



# Feedback

- Please give me your feedback
  - Email: [cropj@eecs.oregonstate.edu](mailto:cropj@eecs.oregonstate.edu)
  - Text: (541) 250-0253
  - Twitter: @JoeCrop