

## case Statement

- ▶ Nesting if past two levels is error prone and possibly inefficient.
- ▶ case excels when many tests are performed on the same expression.
- ▶ case works well for muxes, decoders, and next state logic.

### CASE Statement Structure


```
always τ  
case (case_expression)  
  case_item1 : case_item_statement1;  
  case_item2 : case_item_statement2;  
  case_item3 : case_item_statement3;  
  case_item4 : case_item_statement4;  
  default   : case_item_statement5;  
endcase
```

case is shorthand to describe a complicated if/then/else structure.
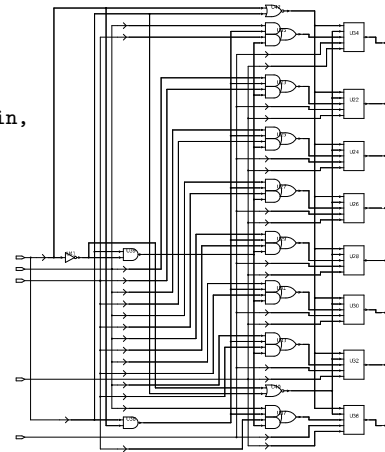
## case Statement

```
// "full case" case statement
module case1 (
    input    [7:0] a_in, b_in, c_in, d_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
            2'b11 : d_out = d_in;
        endcase
endmodule
```



## case Statement


Is the simulation correct?

```

// "full case" case statement
module case1 (
    input    [7:0] a_in, b_in, c_in, d_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
            2'b11 : d_out = d_in;
        endcase
endmodule

```

 

## case Statement

Use default case to propagate "x"

```
// "full case" case statement
module case1 (
    input    [7:0] a_in, b_in, c_in, d_in,
    input    [1:0] sel,
    output reg [7:0] d_out);


    always_comb
        case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
            2'b11 : d_out = d_in;
            default : d_out = 8'bx;
        endcase
endmodule
```

/case1/a_in	10								
/case1/b_in	20								
/case1/c_in	30								
/case1/d_in	40								
/case1/sel	0	1	2	3				X	
/case1/d_out	10	20	30	40				xx	
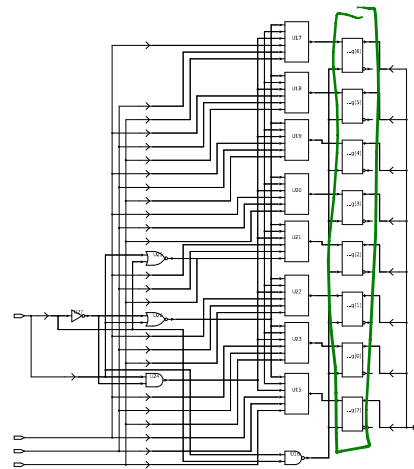
## case Statement

```
//incomplete case statement
module case2 (
    input    [7:0] a_in, b_in, c_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
        endcase
endmodule
```



Inferred memory devices in process in routine case2 line 6 in file 'case2.sv'.


Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
d_out_reg	Latch	8	Y	N	N	N	-	-	-

Warning: Netlist for always\_comb block contains a latch. (ELAB-974)  
Presto compilation completed successfully.
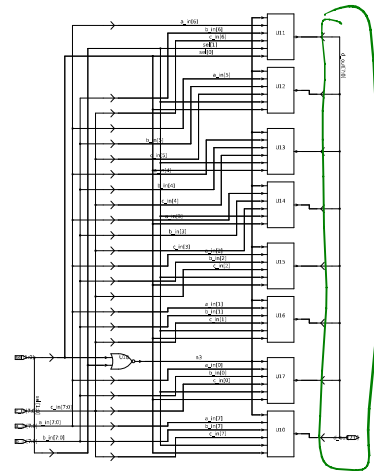
## case Statement

```
//incomplete case statement
//with default case_item
module case2 (
    input    [7:0] a_in, b_in, c_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
            default : d_out = 8'bx;
        endcase
endmodule
```



Does RTL and gate simulation differ when `sel = 2'b11`?

## case Statement


## System Verilog priority Modifier

- ▶ SystemVerilog introduced two case and if statement modifiers
  - ▶ priority
  - ▶ unique
- ▶ Both give information to synthesis to aid optimization.
- ▶ Both are assertions (simulation error reporting mechanisms)
- ▶ Both imply that there is a `case_item` for all the possible legal values that `case_expression` might assume.
- ▶ Priority
  - ▶ Priority tells the simulator that if all is well, you will find a match
  - ▶ If a match is not found at run-time, emit an error or warning.
  - ▶ Since all legal combinations are listed, synthesis is free to optimize any other unlisted `case_items` since they are effectively "don't-cares".
  - ▶ Priority does not guarantee removal of unintended latches.
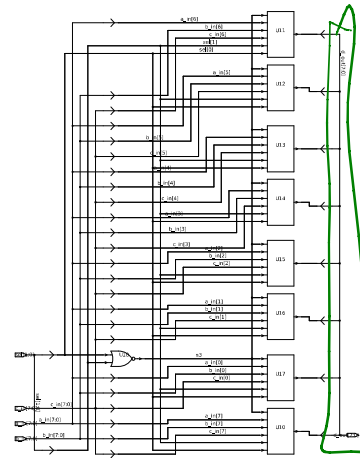
## case Statement

```
//incomplete case statement
//with systemverilog priority modifier
module case2 (
    input    [7:0] a_in, b_in, c_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        priority case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
        endcase
endmodule
```



Warning: case2.sv:7: Case statement marked priority does not cover all possible conditions. (VER-504)



## case Statement


System Verilog priority Modifier

- ▶ OK, so what happens in simulation with 2'b11 ?
- ▶ No x propagation in RTL simulation, but warning is emitted
- ▶ Go back, fix the error that caused the unallowed case to occur.
- ▶ After fixing, the RTL and gate simulation should match.
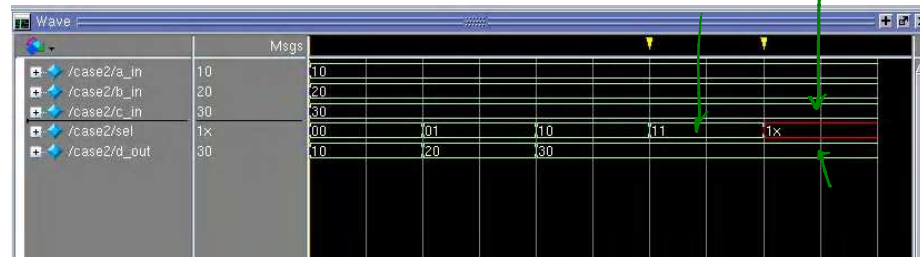
## case Statement

```
//incomplete case statement
//with systemverilog priority modifier
module case2 (
    input    [7:0] a_in, b_in, c_in,
    input    [1:0] sel,
    output reg [7:0] d_out);

    always_comb
        priority case (sel)
            2'b00 : d_out = a_in;
            2'b01 : d_out = b_in;
            2'b10 : d_out = c_in;
        endcase
endmodule
```



```
** Warning: (vsim-8315) case2.sv(7): No condition is true in the unique/priority if/case statement.
** Warning: (vsim-8315) case2.sv(7): No condition is true in the unique/priority if/case statement.
```

## case Statement

### System Verilog priority Modifier

- ▶ Bottom line...
  - ▶ If case is full, use default expression.
  - ▶ If case is not full, use priority modifier.

## casez Statement

- ▶ casez is a special version of the case expression
- ▶ Allows don't care bits in the comparison
- ▶ Uses ? or Z values as don't care instead of as a logic value (weird!)
- ▶ Recommendation: use "?" as don't care
- ▶ Use caution when using this statement


### casez Example

```
module interrupt_ctl1 (  
    output      reg    int2, int1, int0,  
    input  [2:0]      irq      );  
  
    always_comb begin  
        {int2, int1, int0} = 3'b0; //default  
        casez (irq)  
            3'b1?? : int2 = 1'b1;  
            3'b?1? : int1 = 1'b1;  
            3'b??1 : int0 = 1'b1;  
        endcase  
    end  
endmodule
```

## casez Statement
 
### casez Example

```
module interrupt_ctl1 (  
    output reg int2, int1, int0,  
    input [2:0] irq );  
    always_comb begin  
        {int2, int1, int0} = 3'b0; //default  
        casez (irq)  
            3'b1?? : int2 = 1'b1;  
            3'b?1? : int1 = 1'b1;  
            3'b??1 : int0 = 1'b1;  
        endcase  
    end  
end
```



## casez Statement


## Parallel or Unique encoding

- ▶ If the irq bus has any of the values: 3'b011, 3'b101, 3'b110 or 3'b111, more than one case item could match the irq value.
- ▶ This is known as a non-parallel case statement.
- ▶ Synthesis will produce a priority encoder structure.
- ▶ If code could be rewritten to have parallel or unique case items, no priority structure would be needed. Thus, faster/smaller implementation.
- ▶ We indicate this situation with the modifier unique.

## casez Statement
 
### Parallel or Unique Encoding

```
module interrupt_ctl2a (  
    output reg    int2, int1, int0,  
    input         [2:0] irq );  
    always_comb begin  
        {int2, int1, int0} = 3'b0; //default  
        unique casez (irq)  
            3'b1?? : int2 = 1'b1;  
            3'b01? : int1 = 1'b1;  
            3'b001 : int0 = 1'b1;  
        endcase  
    end  
end
```



SYNTHESIS RESULTS ARE INCORRECT!

## casez Statement

Now what?

- ▶ Further work has shown unique to be of at most little benefit.
- ▶ I only got it to work properly once.
- ▶ Synthesis does not stick strictly to priority encoding, its smarter.
- ✎▶ Using unique, I get about 10% decrease in delay and area at best.
- ▶ At this point, until I can bet a better handle on it, avoid unique.



## casex Statement

- ▶ One more case expression exists: `casex`.
- ▶ Can be useful for testbenches.
- ▶ Current recommendations are to not use it in synthesizable code.

## Quiz

1) Number Representation

$y[1:0]$

$$y = 3'b010 \longrightarrow 10$$

signed numbers

0101\_0111\_1111\_0000

2) logical vs. Bitwise

$\rightarrow$   $\begin{matrix} 11 \\ \&\& \end{matrix}$  ,  $\begin{matrix} 1 \\ \& \end{matrix}$   $\neq$

! ~

---

3) always block  
always\_comb