 


Mealy State Machines


- ▶ Mealy state machine outputs are formed by present state and input



- ▶ The structure and operation is identical to a Moore machine except for how the output is formed
- ▶ The machine may also have Moore-type outputs


Mealy State Machines

 - ▶ Mealy outputs are best to stay away from unless a special situation requires it
- ▶ Timing can be tricky to track as flip-flop Q outputs may go through two stages of combo logic prior to the next D-input.
- ▶ At synthesis time, special care must be taken to constrain this special signal



Mealy State Machines

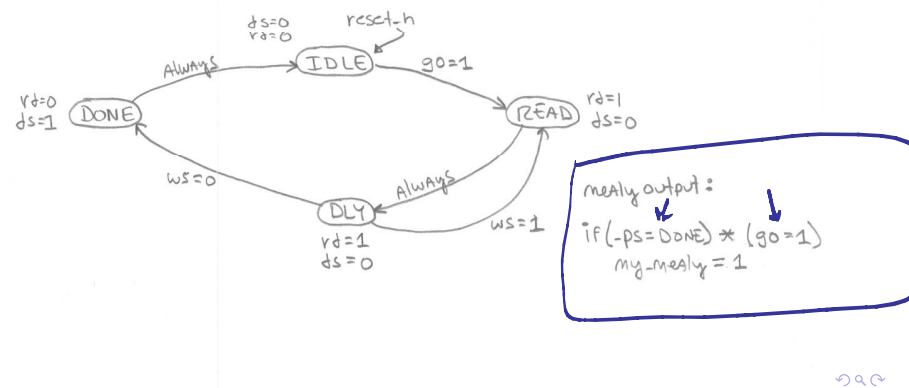
- ▶ Mealy state machine diagrams best show output formation outside the state diagram
- ▶ Simply write the mealy equation below the state diagram and clearly indicate that it is a mealy output



Mealy State Machines

- ▶ Mealy state machine coding
 - ▶ Mealy outputs may be formed inside most any state machine
 - ▶ The Mealy output is formed in the case/if expression
 - ▶ The output is asserted under a state qualified by an if

```
module mealy_noglitch ( output rd, ds,  
                      output reg my_mealy,  
                      input  go, ws, clk, reset_n);  
  
  enum reg [3:0]{ .....  
  always_ff @(posedge clk, .....  
  always_comb begin  
    no_glitch_ns = XX;  
    my_mealy = 1'b0; //default output  
    case (no_glitch_ps)  
      IDLE : if (go) no_glitch_ns = READ;  
      else  : no_glitch_ns = IDLE;  
      READ : no_glitch_ns = DLY;  
      DLY  : if (!ws) no_glitch_ns = DONE;  
      else  : no_glitch_ns = READ;  
      DONE : begin  
                no_glitch_ns = IDLE;  
                if (go) my_mealy = 1'b1;  
            end  
    endcase  
  end  
end
```

 

Mealy State Machines

► The whole enchilada

```
module mealy_noglitch ( output rd, ds,
                      output reg my_mealy,
                      input  go, ws, clk, reset_n);


enum reg [3:0]{
    IDLE = 4'b00_00,
    READ = 4'b01_01,
    DLY  = 4'b01_10,
    DONE = 4'b10_11,
    XX   = 'x} no_glitch_ns, no_glitch_ps;

always_ff @(posedge clk, negedge reset_n)
    if (!reset_n) no_glitch_ps <= IDLE;
    else         no_glitch_ps <= no_glitch_ns;

always_comb begin
    no_glitch_ns = XX;
    my_mealy = 1'b0; //default output
    case (no_glitch_ps)
        IDLE : if (go) no_glitch_ns = READ;
        else    no_glitch_ns = IDLE;
        READ : no_glitch_ns = DLY;
        DLY  : if (!ws) no_glitch_ns = DONE;
        else    no_glitch_ns = READ;
        DONE : begin
                    no_glitch_ns = IDLE;
                    if (go) my_mealy = 1'b1;
                end
    endcase
end
assign {ds,rd} = no_glitch_ps[3:2];
endmodule
```


Mealy State Machines

- Synthesis results

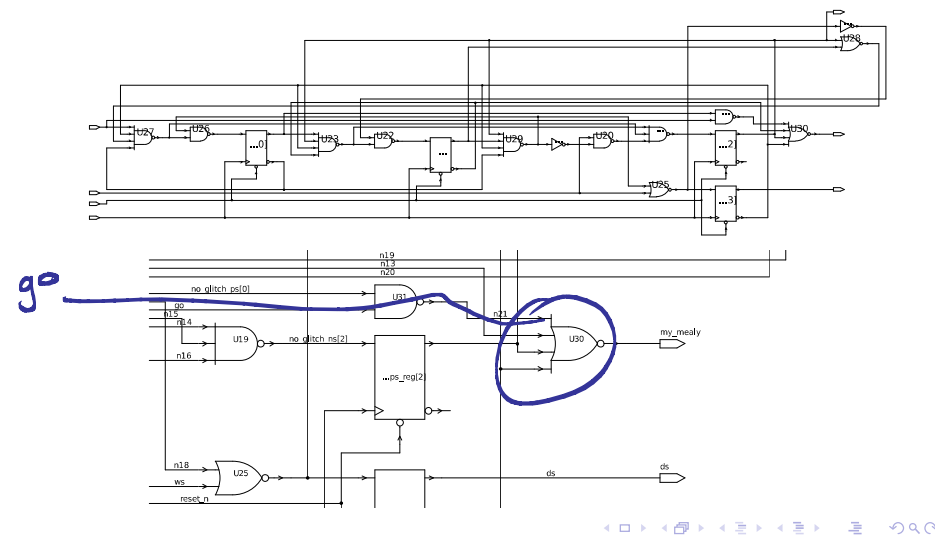

Write both a mealy and moore machine to find the pattern "010" in a serial string of binary inputs.


Input: 0 0 1 1 0 1 0 1 0 1

 

Write both a mealy and moore machine to find the pattern "010" in a serial string of binary inputs.

Input: 0 0 1 1 0 1 0 1

Mealy

 

$f = F2 \& in$